

Sequential Logic

Usage and Copyright Notice:

Copyright 2005 © Noam Nisan and Shimon Schocken

This presentation contains lecture materials that accompany the textbook “The Elements of Computing Systems” by Noam Nisan & Shimon Schocken, MIT Press, 2005.

We provide both PPT and PDF versions.

The book web site, www.idc.ac.il/tecs , features 13 such presentations, one for each book chapter. Each presentation is designed to support about 3 hours of classroom or self-study instruction.

You are welcome to use or edit this presentation as you see fit for instructional and non-commercial purposes.

If you use our materials, we will appreciate it if you will include in them a reference to the book’s web site.


If you have any questions or comments, you can reach us at tecs.ta@gmail.com

Sequential VS combinational logic


- **Combinational devices:** operate on data only; provide calculation services (e.g. Nand ... ALU)
- **Sequential devices:** operate on data and a clock signal; as such, contain *state* and can be made to provide storage and synchronization services
- Sequential devices are sometimes called “clocked devices”
- The low-level behavior of clocked / sequential gates is tricky
- The good news:
 - All sequential chips can be based on one low-level sequential gate, called “data flip flop”, or DFF
 - The complex clock-dependency details can be encapsulated at the low-level DFF level
 - All the higher-level sequential chips can be built on top of the DFF using combinational logic only.

Lecture plan

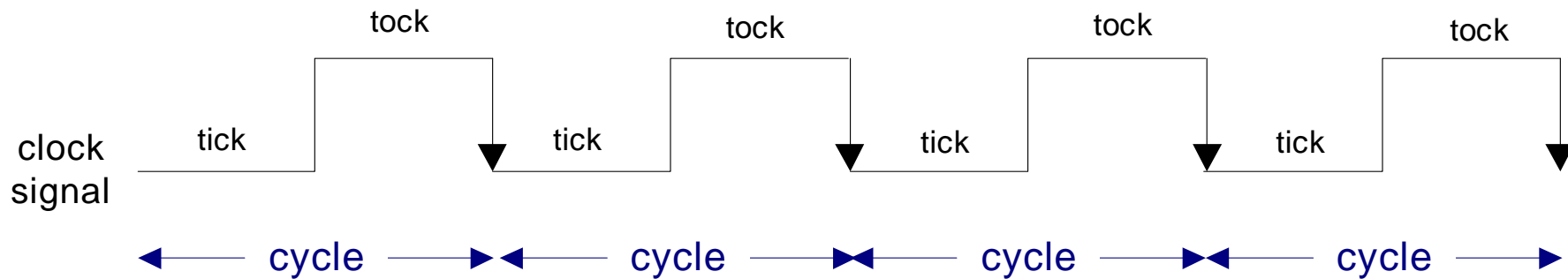
- Clock
- A hierarchy of memory chips:
 - Flip-flop gates
 - Binary cells
 - Registers
 - RAM
- Counters
- Perspective.



 - In our jargon, a clock cycle = *tick*-phase (low), followed by a *tock*-phase (high)
- In real hardware, the clock is implemented by an oscillator
- In our hardware simulator, clock cycles can be simulated either
 - Manually, by the user, or
 - "Automatically," by a test script.




 
- A fundamental state-keeping device
- For now, let us not worry about the DFF *implementation*
- Memory devices are made from numerous flip-flops, all regulated by the same master clock signal
- Notational convention:





1-bit register (we call it “Bit”)

Objective: build a storage unit that can:

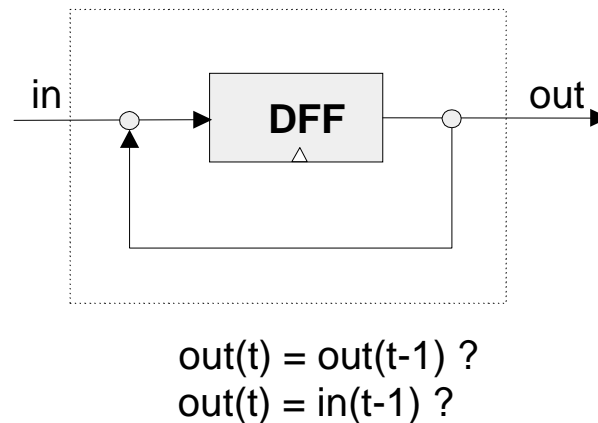 - (a) Change its state to a given input
- (b) Maintain its state over time (until changed)




Won't work

  


OK

Interface

 


if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)

Implementation

 


- Load bit
- Read logic
- Write logic

 

if load($t-1$) then out(t)=in($t-1$)
else out(t)=out($t-1$)

1-bit register

 

if load($t-1$) then out(t)=in($t-1$)
else out(t)=out($t-1$)

w-bit register


- Register's width: a trivial parameter
- Read logic
- Write logic

Relevant topics from the HW simulator tutorial:

- Clocked chips: When a clocked chip is loaded into the simulator, the clock icon is turned on, and the user can use it to control the clock
- Built-in chips:
 - feature a standard HDL interface yet a Java implementation
 - Provide behavioral simulation services
 - May have GUI effects.


Random Access Memory (RAM)

HW
simulator
demo

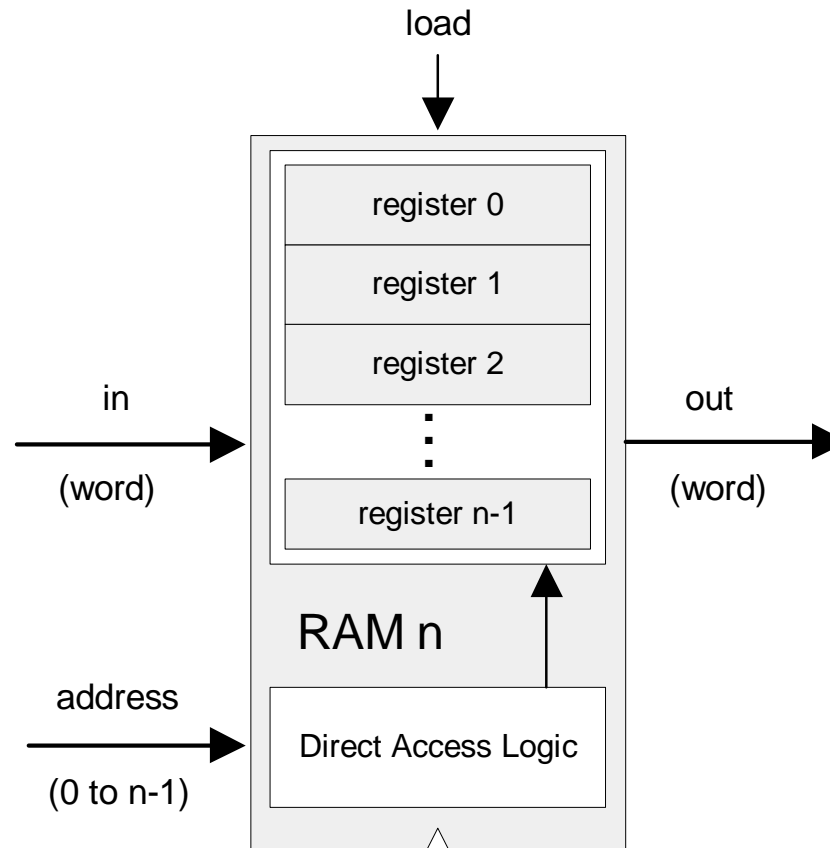

- Read logic
- Write logic.

RAM interface

 


```
Chip name:  RAMn  // n and k are listed below
Inputs:     in[16], address[k], load
Outputs:    out[16]
Function:    out(t) = RAM[address(t)](t)
             If load(t-1) then
                 RAM[address(t-1)](t) = in(t-1)
Comment:    "=" is a 16-bit operation.
```

The specific RAM chips needed for the Hack platform are:

<u>Chip name</u>	<u>n</u>	<u>K</u>
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14


RAM anatomy

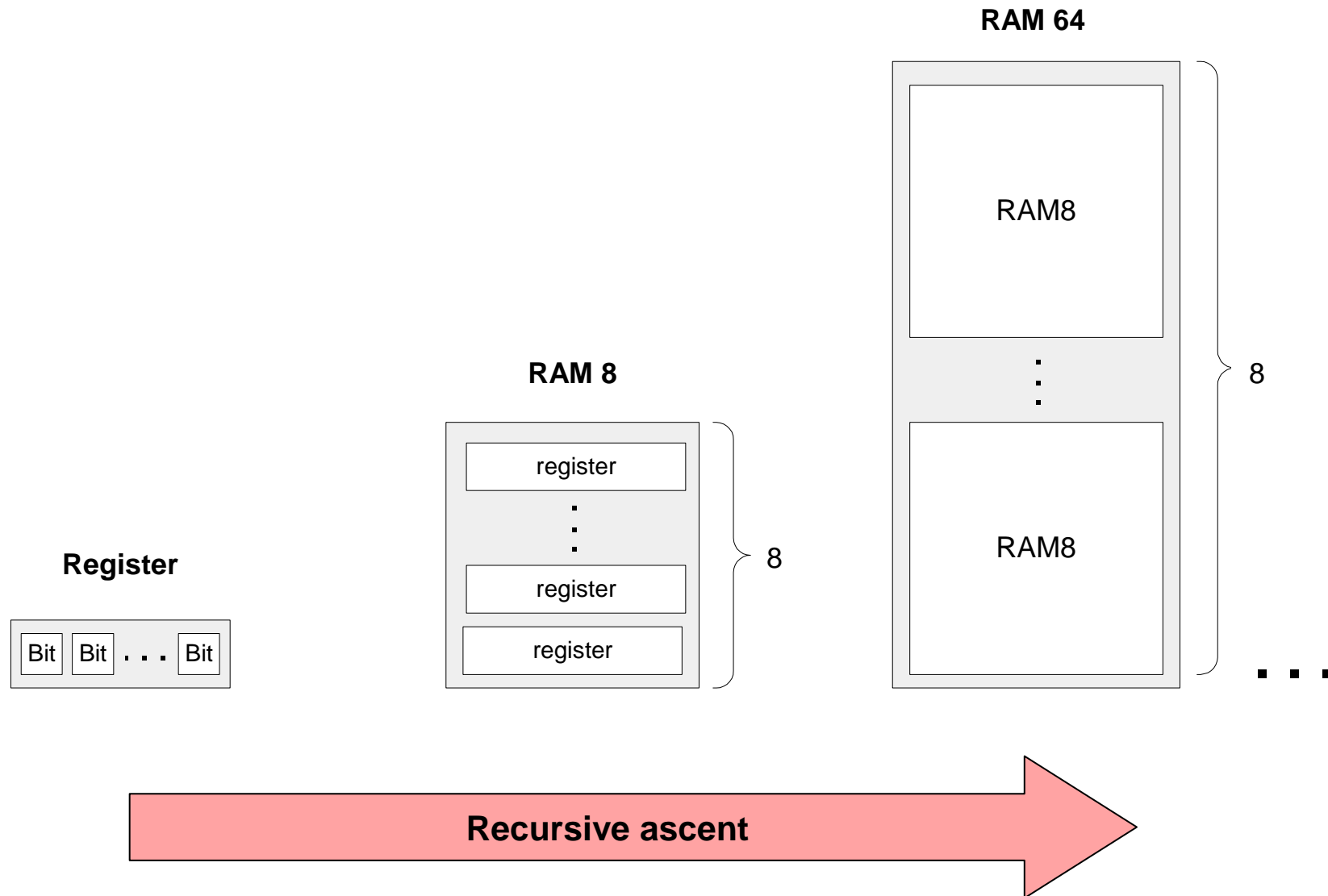

Counter

Needed: a storage device that can:

 - (a) set its state to some base value
- (b) increment the state in every clock cycle
- (c) maintain its state (stop incrementing) over clock cycles
- (d) reset its state




```
If reset(t-1) then out(t)=0
  else if load(t-1) then out(t)=in(t-1)
    else if inc(t-1) then out(t)=out(t-1)+1
      else out(t)=out(t-1)
```

- Typical function: *program counter*
- Implementation: register chip + some combinational logic.


Recap: Sequential VS combinational logic

Combinational chip

 


$out = \text{some function of } (in)$

Sequential chip

 


$out(t) = \text{some function of } (in(t-1), out(t-1))$

Time matters

 

 - During a tick-tock cycle, the **internal states** of all the clocked chips are allowed to change, but their **outputs** are "latched"
- At the beginning of the next cycle, the **outputs** of all the clocked chips in the architecture **commit** to the new values.



Implications:

- Challenge: propagation delays
- Solution: clock synchronization
- Cycle length and processing speed.

Perspective

- All the memory units described in this lecture are standard

- Typical memory hierarchy

- SRAM ("static"), typically used for the cache
- DRAM ("dynamic"), typically used for main memory
- Disk

(Elaborate caching / paging algorithms)

- A Flip-flop can be built from Nand gates
- But ... real memory units are highly optimized, using a great variety of storage technologies.

